

Assignment 2

CENG 355

The propagation delays of the flip-flops, multiplexors, decoders, memories, adders and gates used in the very simple 2-instruction computer that was discussed in class are 10ns. The setup time for the flip-flops is 5 ns. How fast can the computer be clocked?

What is the CPI for the computer?